 


State Diagram



Idea

It's pretty simple actually where the I go to the next states whenever I find a bit from the sequence as you can see sometimes I don't find the expected value from the pattern so I keep waiting for it in some cases and some other cases I go back again to the first state and start over.

Why do I go to C₁₁ if I got the last one wrong?

To follow the overlapping technique where if I find 11011 the 11 at the end can be useful if 11011 01000 you could see here it's better to search for "010" I already have the 11 from the previous pattern that is purely overlapping if I was non-overlapping no pattern will be found because they wouldn't consider the pattern from the previous iteration.

Code

```
module SeqDetect_FSM(
    input clk,
    input reset,
    input Bit_Stream,
    output reg Out_BitStream
);
parameter State_Reg_Width = 3;
wire [State_Reg_Width-1:0] S_0 = 3'b000,
    S_1 = 3'b001,
    S_11 = 3'b010,
    S_110 = 3'b011,
    S_1101 = 3'b100; //Had to define them as wire to run in
                      //Modelsim

    reg [State_Reg_Width-1 : 0] Next_State , Curr_State;

    integer i = 0;
    always @(posedge clk ) begin
        if(reset)begin
            Curr_State <= S_0;
        end
        else begin
            Curr_State <= Next_State;
            i = i+1;
        end
    end

    always @(*) begin
        Out_BitStream = 0;
        case (Curr_State)

            S_0:begin
                if(Bit_Stream == 1)begin
                    Next_State = S_1;
                end
                else begin
                    Next_State = S_0;
                end
            end

            S_1:begin
                if(Bit_Stream == 1)begin
                    Next_State = S_11;
                end
                else begin
                    Next_State = S_0;
                end
            end

            S_11:begin
                if(Bit_Stream == 0)begin
                    Next_State = S_110;
                end
                else begin
                    Next_State = S_11;
                end
            end

            S_110:begin
                if(Bit_Stream == 1)begin
                    Next_State = S_1101;
                end
                else begin
                    Next_State = S_0;
                end
            end

            S_1101:begin
                if(Bit_Stream == 0)begin
                    Out_BitStream = 1;
                    Next_State = S_0;
                    $display("Pattern Found at iteration %d",i);
                end
                else begin
                    Out_BitStream = 0;
                    Next_State = S_11;
                end
            end
        endcase
    end

endmodule
```

```
module PatternDetect_TB ();

    reg clk_TB;
    assign clk_TB = 1;
    always #(50) clk_TB = ~clk_TB; // I wrote 50 since if i define time it gives Error in ModelSim

    reg reset_TB;
    reg Bit_Stream_TB;
    wire Out_BitStream_TB;

    SeqDetect_FSM DUT(.clk(clk_TB) , .reset(reset_TB) , .Bit_Stream(Bit_Stream_TB) ,
    .Out_BitStream(Out_BitStream_TB) );

    //Test: 11011 1010 1 1010 1111010
    task SET_Clear_BIT(input Bit_TB);
    begin
        Bit_Stream_TB = Bit_TB;
        #100
        Bit_Stream_TB = 0;
    end
endtask

initial begin
    reset_TB = 1;
    SET_Clear_BIT(0);
    reset_TB = 0;

    SET_Clear_BIT(1);
    SET_Clear_BIT(1);
    SET_Clear_BIT(0);
    SET_Clear_BIT(1);
    SET_Clear_BIT(1);
    SET_Clear_BIT(1);

    SET_Clear_BIT(1);
    SET_Clear_BIT(0);
    SET_Clear_BIT(1);
    SET_Clear_BIT(0);

    SET_Clear_BIT(1);

    SET_Clear_BIT(1);
    SET_Clear_BIT(0);
    SET_Clear_BIT(1);
    SET_Clear_BIT(0);

    SET_Clear_BIT(1);
    SET_Clear_BIT(1);
    SET_Clear_BIT(1);
    SET_Clear_BIT(1);
    SET_Clear_BIT(0);
    SET_Clear_BIT(1);
    SET_Clear_BIT(0);

    $finish();
end

endmodule
```